

CE 3111.103

Lab 5: BJT Amplifiers – Part II

TA: Jingcheng Liang

**Yu Feng**


Student ID: 2021322786

## Objective


Compare behaviour of CEED with CE configuration. Look at amplifier's response, mid-band gain, and low and high cut-off frequencies.
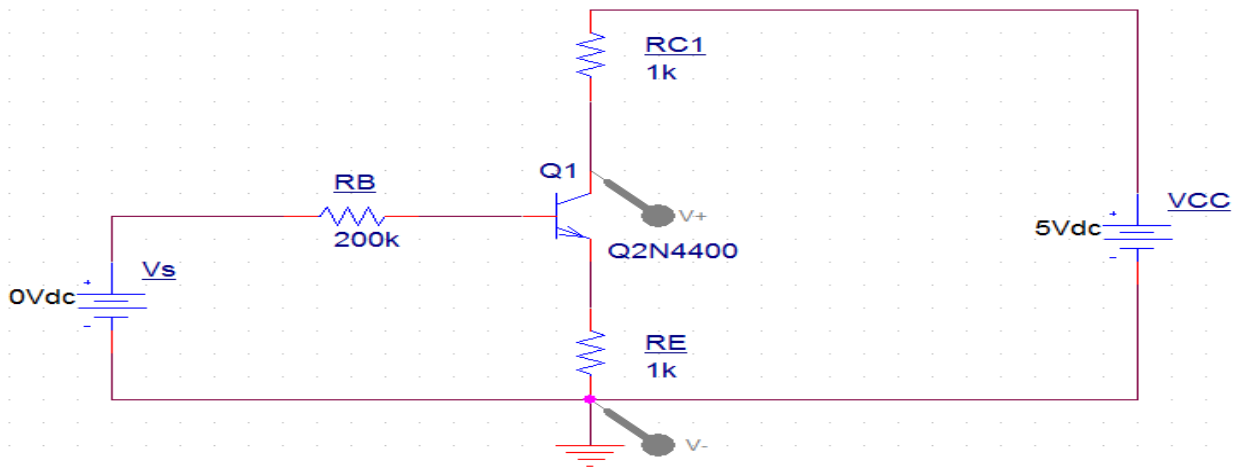
## Experimental Results

- CE with Emitter Degeneration
  - PSpice circuit




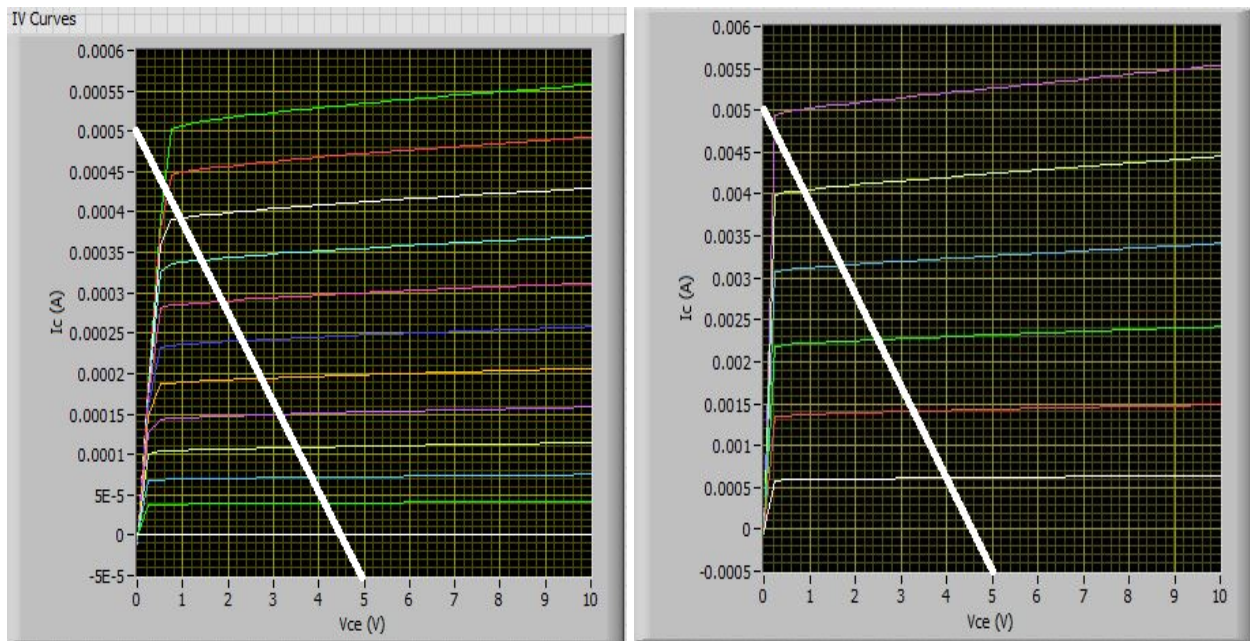2. Load line:  $I_C = \frac{5V - V_C}{10k\Omega}$




- Left: I-V curve of CEED. Right: I-V curve of CE
- The additional Re caused the IC 10 times smaller than without it.

### 3. Transfer function

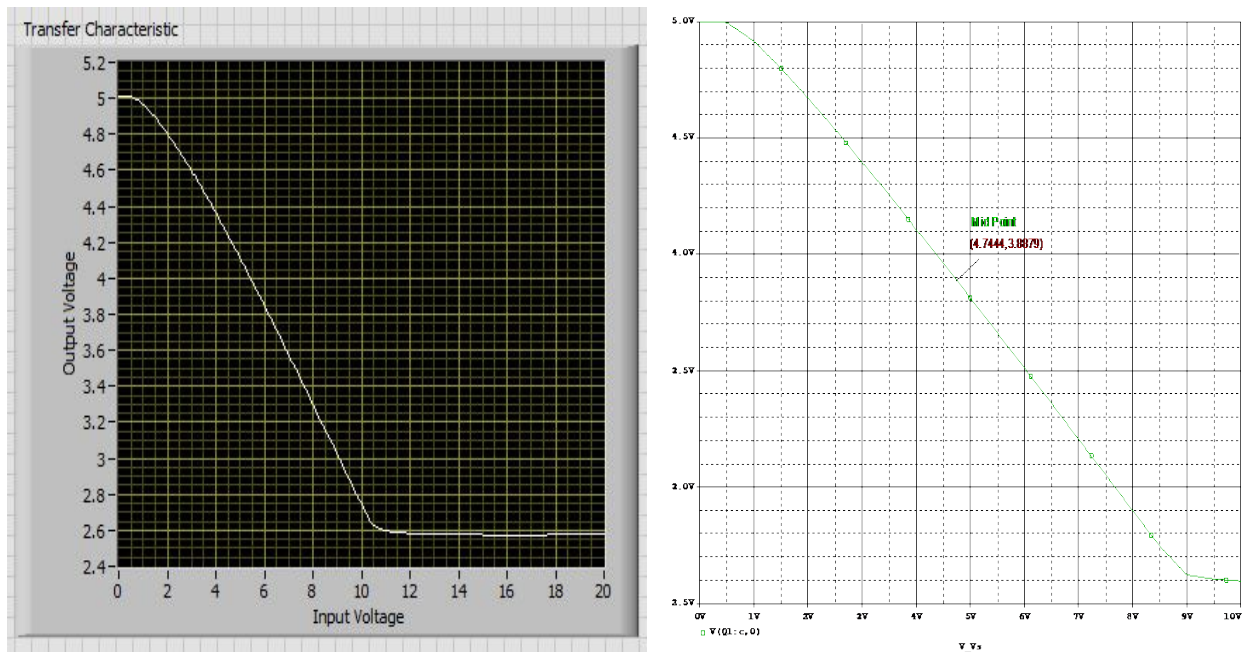


- Left: Experimental result Right: Simulation result
- $(V_{in,min}, V_{out,max}) = (0.6, 4.99)$
- $(V_{in,max}, V_{out,min}) = (10.5, 2.62)$
- $(V_{in,middle}, V_{out,middle}) = (5.55, 3.87)$
- $\text{Gain, experiment} = \frac{3.87 - 4.1}{5.55 - 5} = -0.41818$
- $\text{Gain, Simulation} = -0.2977$

### 4. Small signal Voltage gain

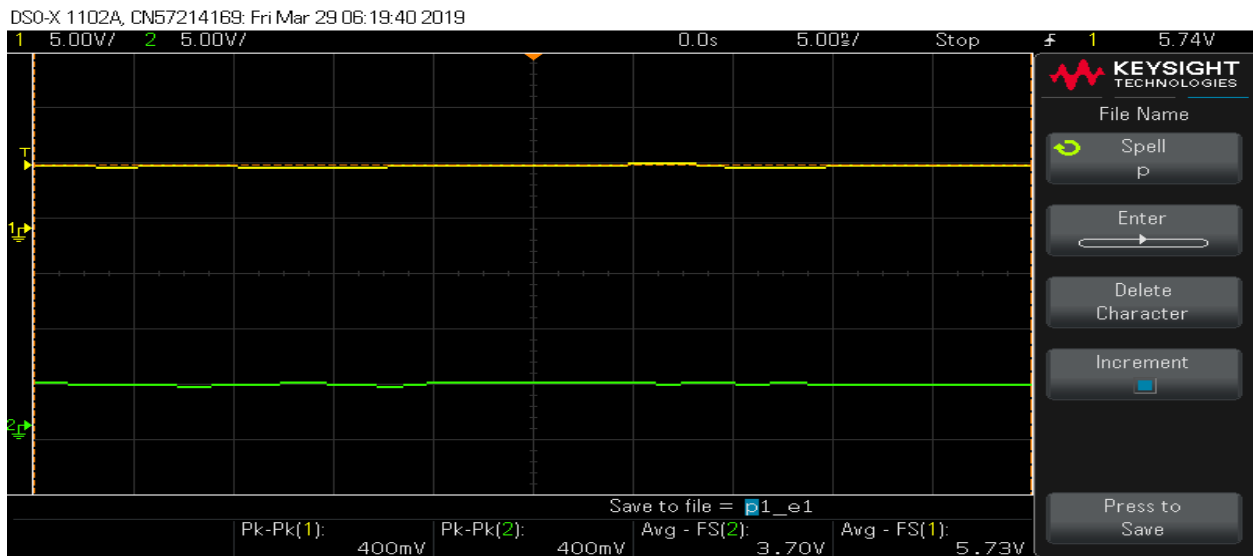

- $\text{AC Gain} = \frac{V_{out}}{V_{in}} = \frac{3.70}{5.73} = 0.64572$


## 5. Clip

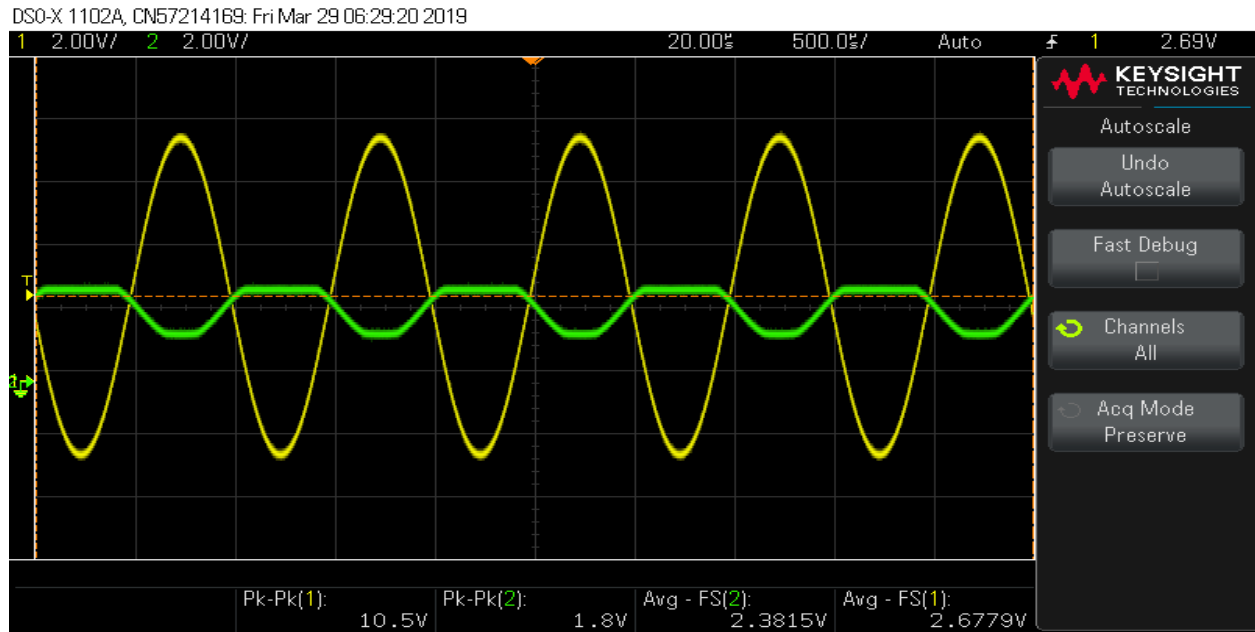


Clipping occurs because of the negative gain characteristic of the amplifier, and the transfer function rules the  $V_{out}$  decreases as  $V_{in}$  increases.

- CE amplifier with bias circuit and AC-coupled I/O

### 1. PSpice circuit

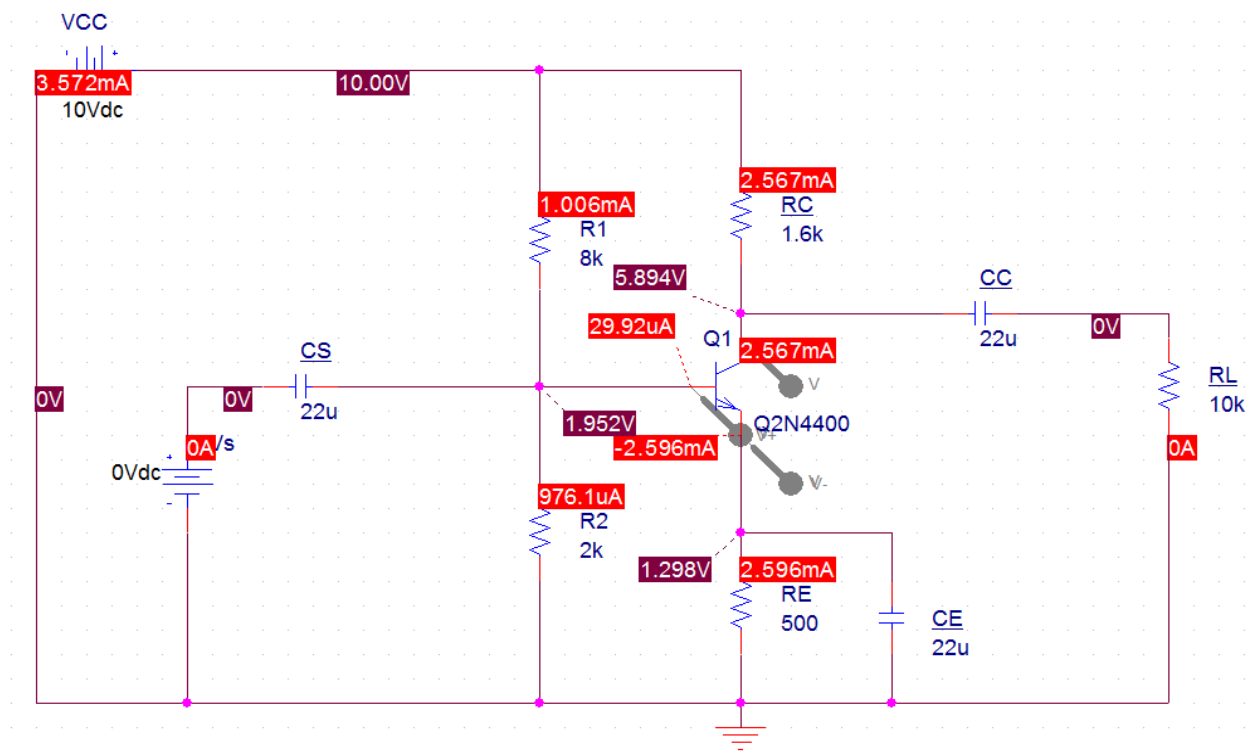


## 2. Small signal voltage gain

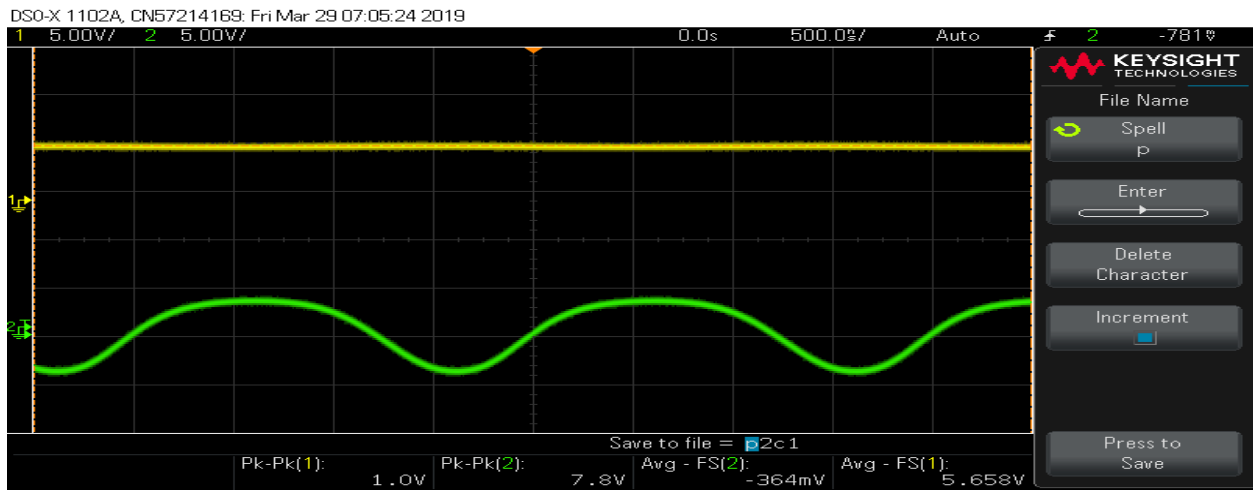


- Gain =  $\frac{V_{out}}{V_{in}} = \frac{-364mV}{5.658V} = -0.06433$
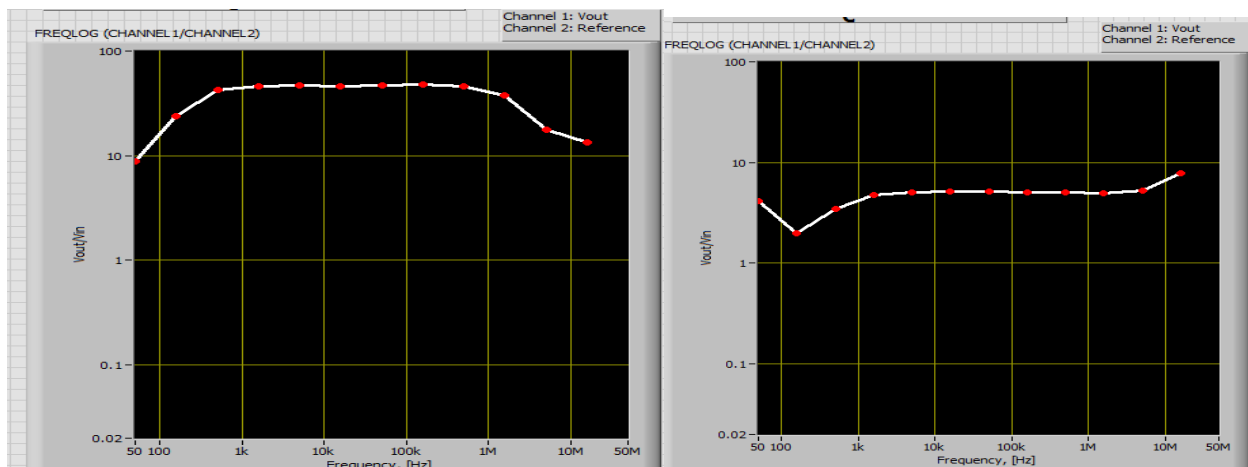
## 3. Bode plots

- Left: Original Right:  $R_L$  reduction



- $C_E$  removed


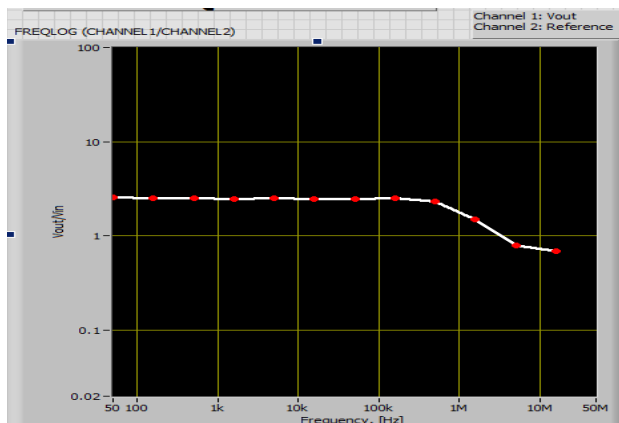


Due to instrumental error, graphs may not be accurate



- When  $R_L$  is small, it dominates the mid-band gain.
- When  $C_E$  is removed,  $R_E$  dominates the mid band gain through  $g_m$ .

## Analysis Question

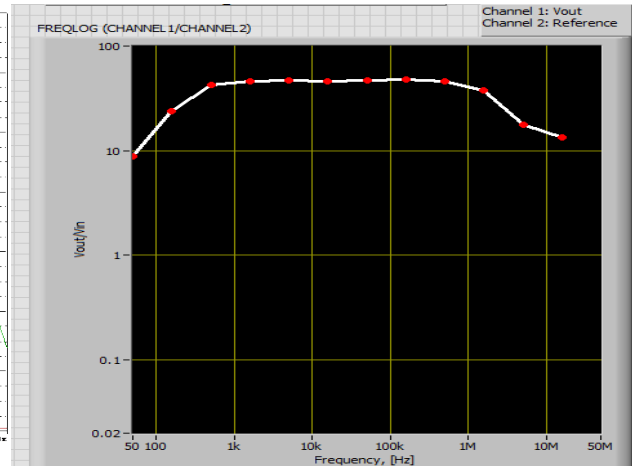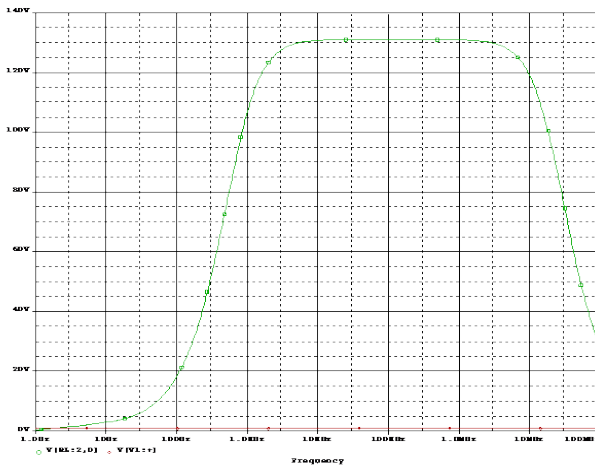1. The additional  $R_E$  caused the output voltage to be smoother. It also decrease the gain a little bit.
2.
  - a. The experimental graph shows only the top part of the actual response.



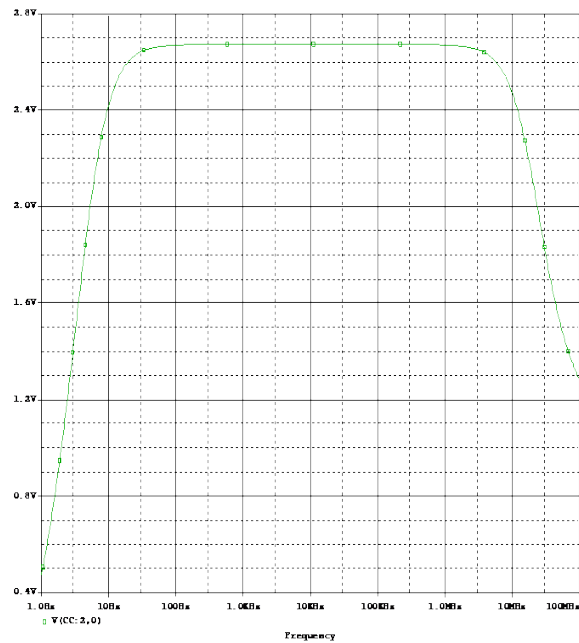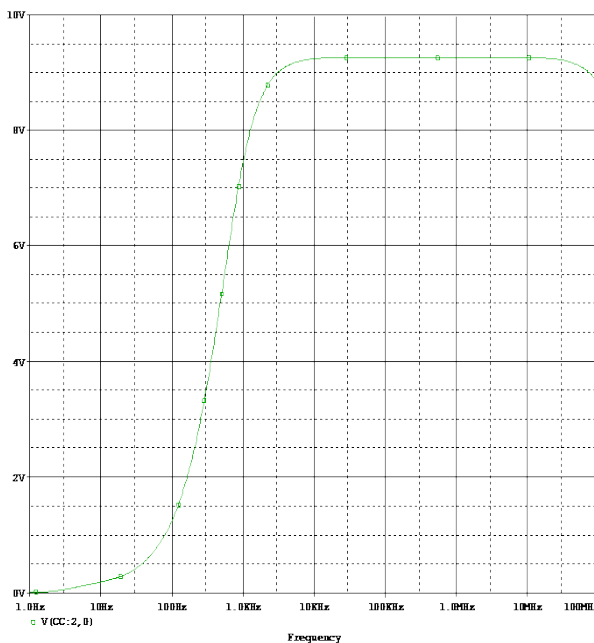- b. Left: smaller  $R_E$  Right: removed  $C_E$ . The simulation has discrepancies to the experimental result due to errors occurred in oscilloscope. The gains from both modification to the amplifier decrease due to the maximum output voltage decrease.



$$c. \quad A_{mid,original} = -\frac{0.19mA}{26mV} \times \frac{1.6k \times 10k}{1.6k + 10k} = -10.0796$$

$$A_{mid,new load} = -\frac{0.19mA}{26mV} \times \frac{1.6k \times 100}{1.6k + 100} = 0.68778$$

Calculation matches measurement.

3. The smaller the  $R_L$ , the smaller the amplifier gain. The bigger the  $R_E$ , the bigger the amplifier gain through  $g_m$ .
4.  $R_E$  affects  $G_m$ ,  $R_{\pi}$  of the small signal model. The effect can be made positive in terms of restricting the output voltage, making it stable.  $R_E$  must be chosen in the FAR region of BJT, so  $V_{CE} > V_{BE}$ . It serves the origin of CEED circuits, which is to stabilize the output.